

Connections Overview:

- First we will connect the two potentiometer vcc pin to 5v in Arduino, Gnd to Gnd pins in Arduino Uno and other pin of gas potentiometer to A0, Temp potentiometer to A1.
- We will connect the buzzer positive to the D8 and negative to the Gnd
- We will connect the Dc motor positive to the pin D9 and negative to the Gnd
- The LED anode is connected to resistor one end and it is connected to the pin D2 and the other to Gnd